
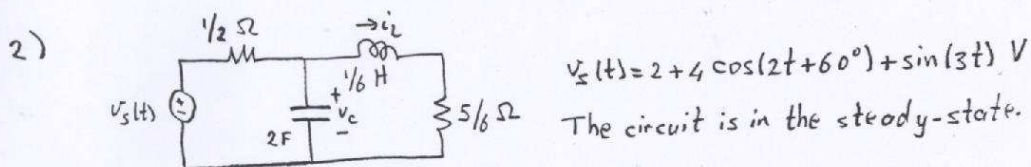


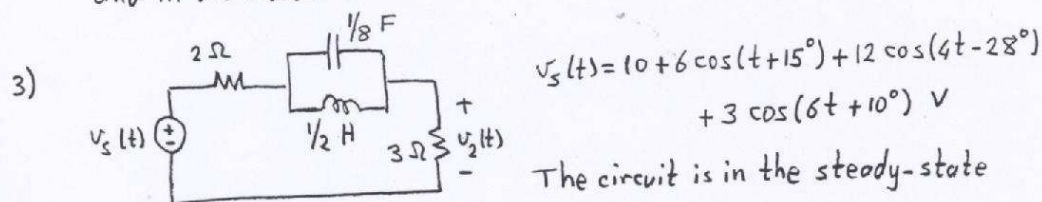
- (a) Find the particular solution when $\omega = 3$ rad/sec.
 (b) Find the homogeneous solution for (i) $K=2$, (ii) $K=3$, (iii) $K=4$,
 (iv) $K=5$, (v) $K=6$.
 (c) For each K value above discuss whether the steady-state is well defined or not. In case the steady-state well defined, find the steady-state solution.
 (d) Find the particular solution when $\omega = 2$ rad/sec and $K=2$. Discuss the existence of the steady-state solution.



- (a) Find $v_c(t)$ and $i_L(t)$.
 (b) Compute the average powers delivered to the resistors, the average power supplied by the source, the average stored energies in the capacitor and in the inductor.




Find $v_2(t)$.

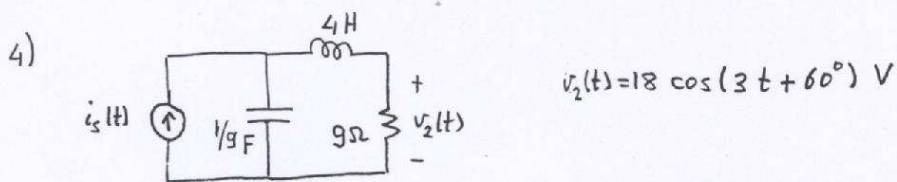


(a) Find $i_s(t)$.

(b) Sketch the phasor diagram.

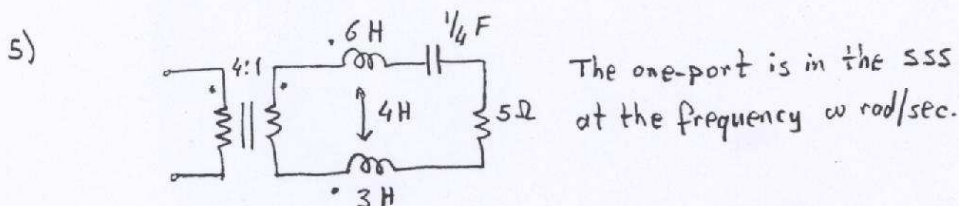

Find the input impedance $Z(j\omega)$.

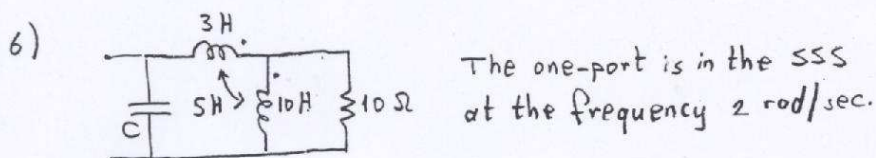
For which values of ω is this one-port resistive? capacitive? inductive?



(a) Find the input admittance $Y = G + jB$ in terms of C .

(b) Define $\delta \triangleq G/|Y|$. Determine the value of C such that

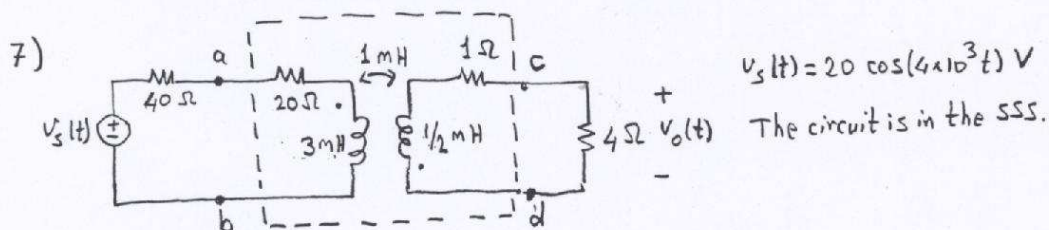(i) $\delta = 1$, (ii) $\delta = 0.8$, $B > 0$, (iii) $\delta = 0.8$, $B < 0$.




(a) Transform the circuit to the phasor domain.

(b) Obtain the chain parameters of the indicated two-port.

(c) Using the chain parameters find the Thevenin equivalent as seen to the left of the terminal pair c-d.

(d) Find $v_o(t)$.

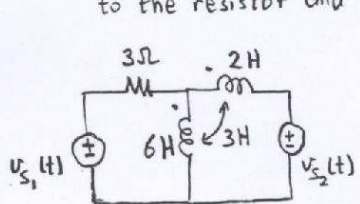
- 8) The circuit is in the steady-state. Compute the average power delivered to the resistor and the average stored energy in the coupled inductor.



$$v_{s1}(t) = 6 \cos(2t) \text{ V}$$

$$v_{s2}(t) = 10 \sin(t + 30^\circ) \text{ V}$$


(a)

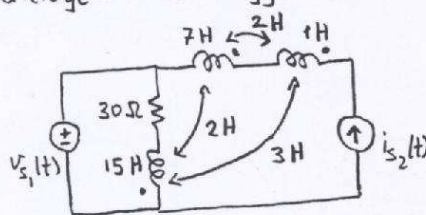

$$v_{s1}(t) = 30 \sin(2t) \text{ V}$$

$$i_{s2}(t) = \frac{\sqrt{3}}{6} \cos(3t - 15^\circ) \text{ A}$$

(b)

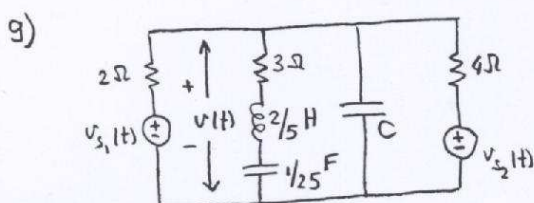


$$v_{s1}(t) = V_{m1} \cos(5t + \theta_1) \text{ V}$$

$$v_{s2}(t) = V_{m2} \cos(12.5t + \theta_2) \text{ V}$$

$$v(t) = \sqrt{2} [60 \cos(5t) + 90 \cos(12.5t)] \text{ V}$$

(a) Compute $P_{3\Omega \text{ avg}}$.

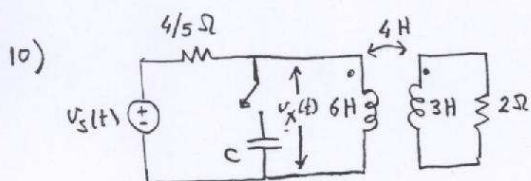(b) The average power supplied by the left source is 2 kW. Compute $P_{2\Omega \text{ avg}}$.




$$v_{s1}(t) = V_m \cos(2t + \theta_s) \text{ V}$$

The circuit is in the SSS.

(a) The switch is open, $V_{x \text{ eff}} = 10 \text{ V}$. Compute $P_{2\Omega \text{ avg}}$ and the average stored energy in the coupled inductor.

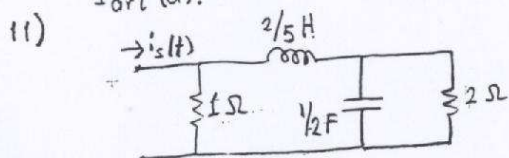(b) The switch is closed, $V_{x \text{ eff}} = 10 \text{ V}$. Determine the value of C so that the average power supplied by the source is 1 W less than that of Port (a).




$$i_s(t) = \sqrt{2} \cos(3t) \text{ A}$$

The circuit is in the SSS.


(a) Find the input impedance Z of the one-port.

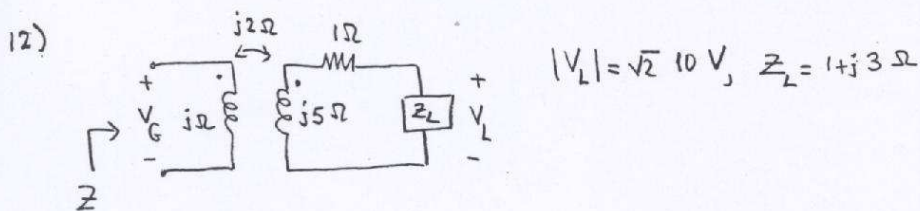(b) Show that $Z I_{s \text{ eff}}^2 = [P_{1\Omega \text{ avg}} + P_{2\Omega \text{ avg}}] + j2 \times 3 \times [E_{L \text{ avg}} - E_{C \text{ avg}}]$.




(a) Find $|V_G|$ and Z .

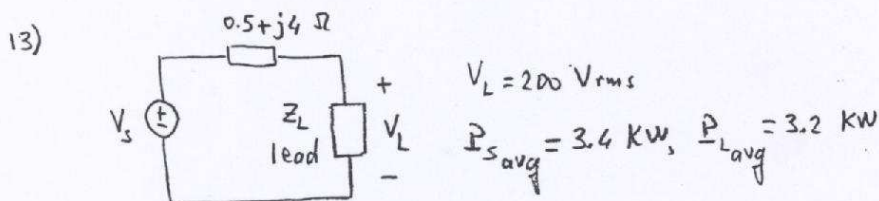(b) Compute the average power delivered to the resistor and the ratio of the average stored energies in the coupled inductor and in Z_L .



Find $V_{s,eff}$.

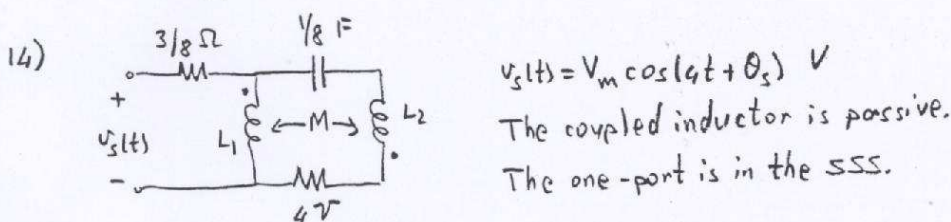


The average power delivered to the $3/8 \Omega$ resistor is 6 W.

The average stored energy in the coupled inductor is 4 J.

The input impedance of the one-port is $Z = Z_m (0.6 - j0.8) \Omega$.

Find V_m and Z_m .

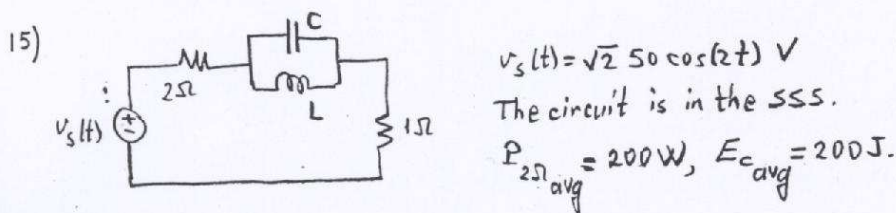

Find $E_{L,avg}$.